


ECE 321 - Qualifier Exam Sample Problems

Semiconductor Physics:


- What is meant by n-type and p-type Silicon?
- For metals, resistance goes up with temperature. For semiconductors, resistance goes down with temperature. Why?

Diodes & the pn junction


- Diodes act like a valve, allowing current to flow from p to n but not the other way. Why?
- Actually, a small amount of current can flow backwards, from n to p. Why?
- A nonlinear device has the following V/I characteristic. It is driven by a 10V source through a 100 Ohm resistor. Sketch the load-line for this circuit and determine V_x and I_x .
- At this operating point, determine a piecewise linear model for R_x

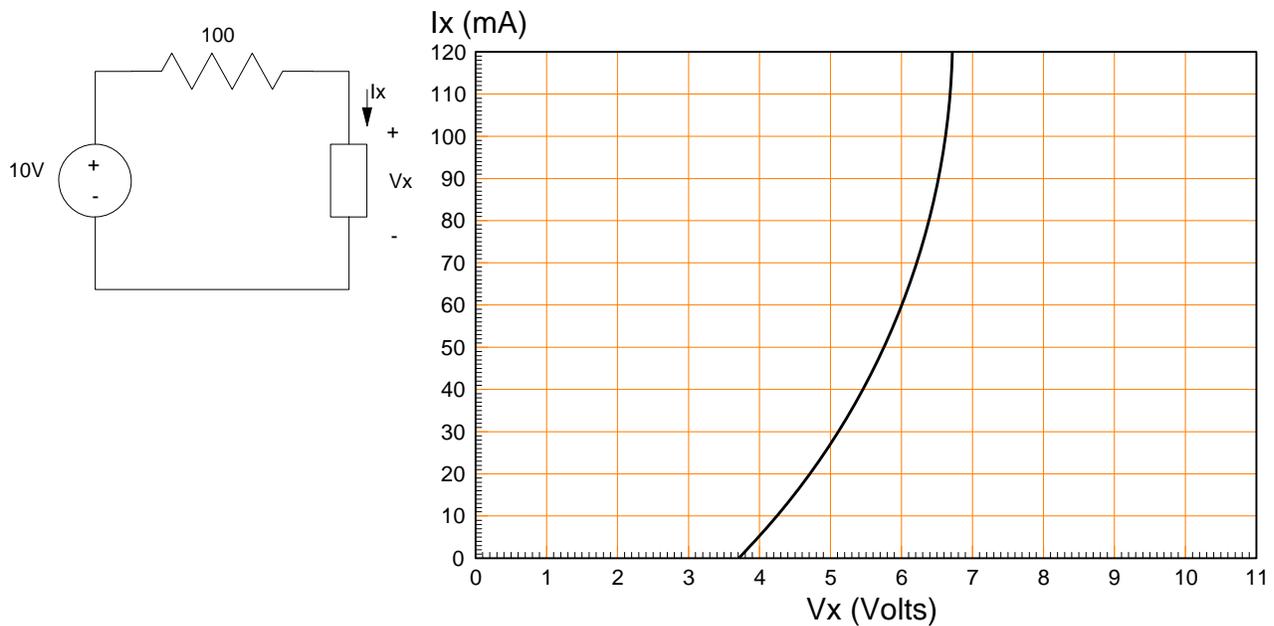

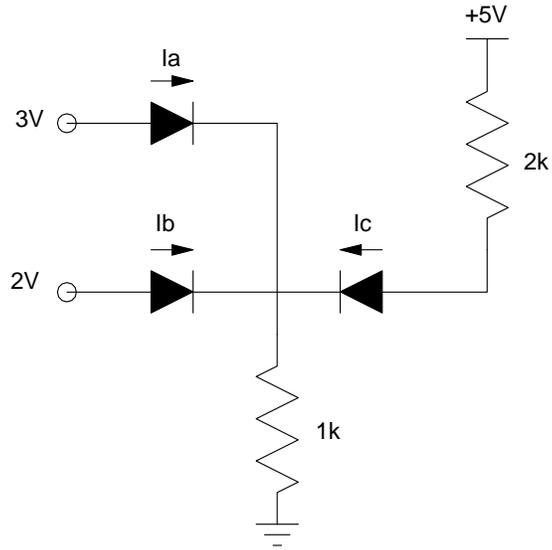- Assume ideal silicon diodes ($V_f = 0.7V$). Determine the currents I_a , I_b , and I_c for the following circuit:





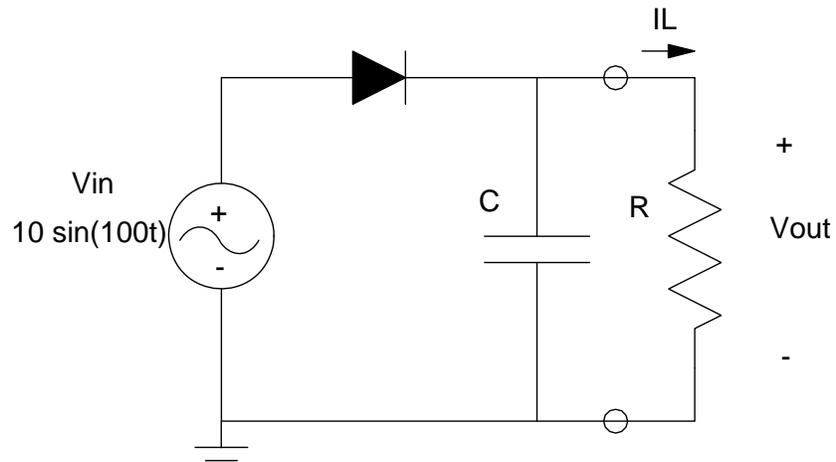
- For the following half-wave rectifier, sketch V_{out} for
 - $R = 1k$ and $C = 0$
 - $R = 1k$ and $C = 1000\mu F$




Transistors:

Assume ideal silicon transistors with a gain of 100 for all problems.

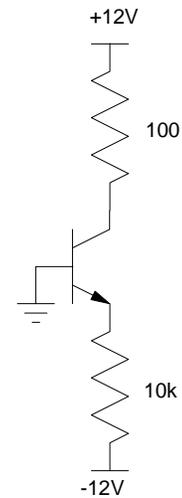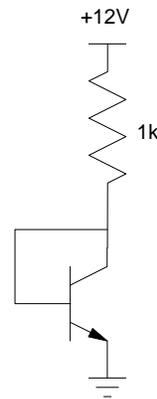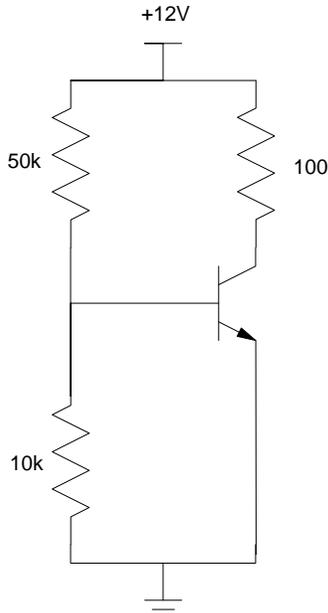- Transistor Switch: Design a circuit with a transistor to meet the following design requirements:
 - Input: 0V or 6V DC signal, capable of driving up to 10mA
 - Output: An 8 Ohm speaker
 - When the input is 0V, no current flows through the speaker
 - When the input is 6V, 6V is applied to the speaker (+/- 0.5V)
- Determine the currents and voltages for the following circuits



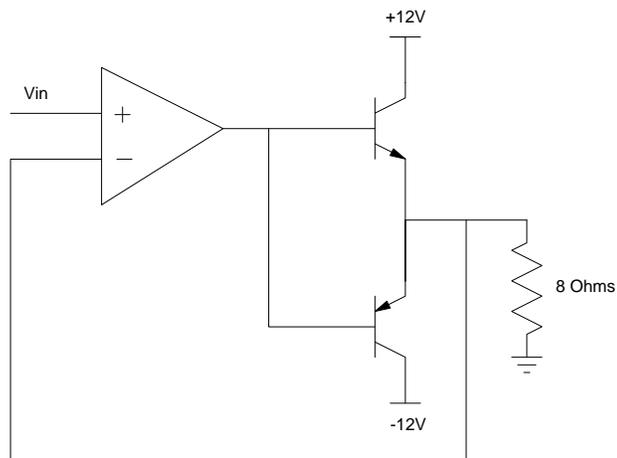- Push-Pull Amplifier: Determine the currents and voltages for
 - $V_{in} = +5V$
 - $V_{in} = -5V$




MOSFET

A MOSFET has the following V/I characteristics. The model for a MOSFET in the active and saturated regions are:

Ohmic:
$$I_{ds} = k_n \left(V_{gs} - V_m - \frac{V_{ds}}{2} \right) V_{ds}$$



Saturated:
$$I_{ds} = k_n (V_{gs} - V_m)^2$$

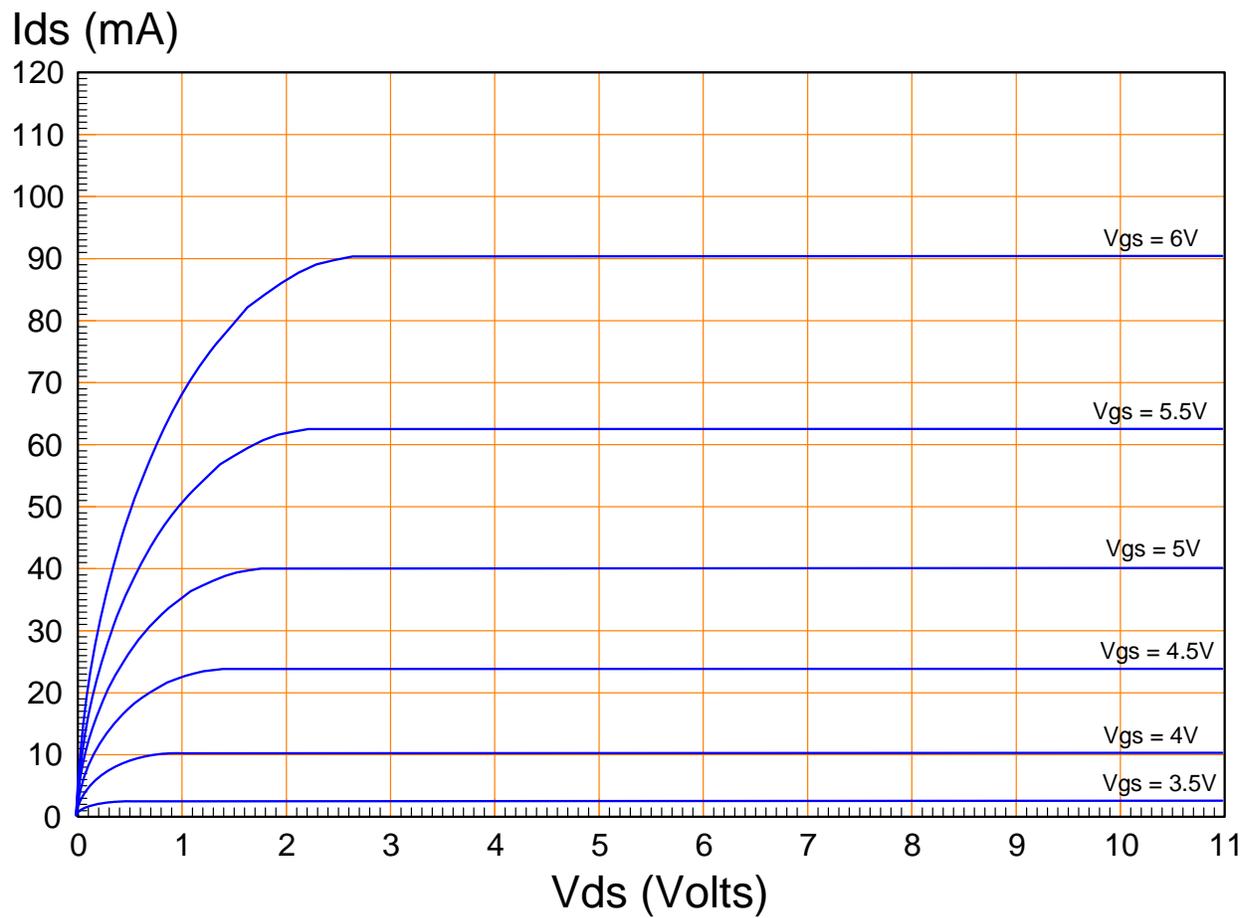- Show on this graph the Ohmic, Saturated, and Off regions
- Determine k_n for this MOSFET





Operational Amplifiers

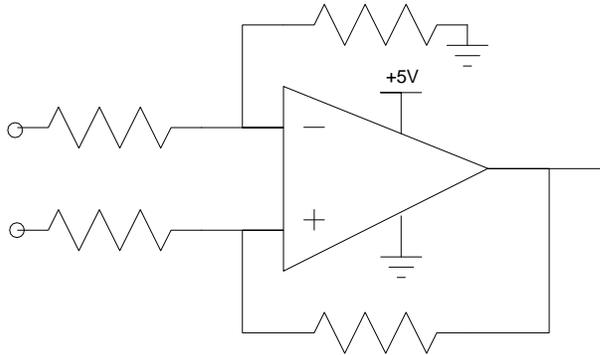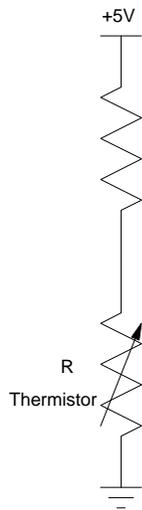- Schmitt Trigger: Find the voltages and resistors so that the output
 - Switches to +5V for $R > 1000$ Ohms, and
 - Switches to 0V for $R < 900$ Ohms



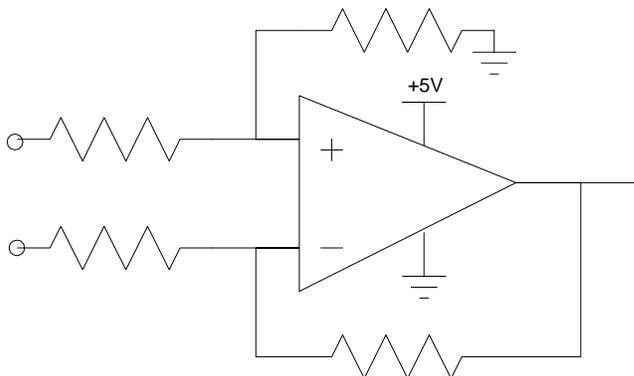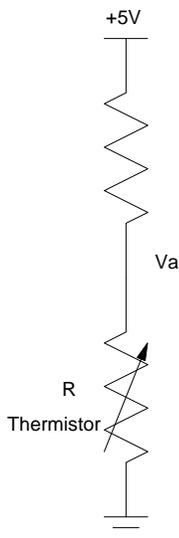- Instrumentation Amplifier: Find the voltages and resistors so that the output is
 - 0V at $R = 900$ Ohms
 - 5V at $R = 1000$ Ohms, and
 - Proportional to R for $900 < R < 1000$ Ohms



- Give N equations to solve for the voltages at the N nodes.

