

For the following exam, **answer 8 out of the following 10 questions**. Each question is worth 12.5 points. **Circle the 8 questions below, Q1-Q10, that you want graded:**

Q1 Q2 Q3 Q4 Q5 Q6 Q7 Q8 Q9 Q10

- 1) The values of the function $F(A, B, C, D)$ are given by the following truth table. Find the minimum sum-of-products (SOP) and product-of-sums (POS) Boolean representations of F , named F_{SOP} and F_{POS} , respectively.

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

- 2) You have only one 7402 IC chip (quad 2-input NOR) available to implement $G = (A+B) \bullet C' \bullet D'$. Show the corresponding logic diagram.

3) $A = 10010110_2$ $B = 1111010_2$

a) If A and B are **unsigned** numbers, what is $A \times B$ in binary? Show the partial products.

b) If A and B are **2^s complement** numbers, what is $A + B$? Show your work.

c) If A and B are **unsigned** numbers, what is $A - B$ using 2^s complement subtraction?
Show your work.


4) a) Convert $+243.647_{10}$ into a **2^s complement** binary number, showing 10 digits in the integer portion and five digits in the fractional portion. Show your work.

b) $8A6.48_{16}$ is a **sign magnitude** number. Convert it into a decimal number. Show your work.

 
- 5) Program the following MUX to implement the function:
 $G = (A+B'+C)(A+C'+D')(B'+C+D')(B+C+D)$. Do not use any additional logic gates.



6a) Draw the output waveforms, Q and Q', for an active-high SR latch. Initially, Q = 0 and Q' = 1.



 b) Show the output waveforms, Q and Q', for an active high clocked SR latch. Initially, Q = 0 and Q' = 1.



- 7) Design a maximum speed, minimal area **CMOS** implementation of a BCD (Binary Coded Decimal) detector, which asserts output, F , when input, $X(3:0)$, is not a valid BCD number.

- 8) Design a positive edge-triggered LM flip-flop using only combinational logic and a basic positive edge-triggered D flip-flop (i.e., D and clk inputs only). The LM flip-flop operates as follows: when $L=0$ the output is loaded with the complement of M (i.e., M'); when $L=1$ and $M=0$ the output is toggled; and when $L=1$ and $M=1$ the output is reset to 0. The resulting design should be optimized for the minimal number of gates and minimal delay.

- 9) Draw the circuit diagram for a 4-bit **2^s complement** counter that operates as follows: if control = 1 then $\text{count}^+ = \text{count}^- + 1_{10}$; else $\text{count}^+ = \text{count}^- - 2_{10}$. An additional output, *OV*, is asserted iff the correct value of count^+ cannot be represented in 4 bits. Use FAs, HAs, and additional logic as necessary, and DFF0 components (i.e., DFFs with a reset-to-0 input) such that the count is resettable to zero.

- 10) For the following state machine, derive the next state and output equations **in minimal SOP form**.
The state variables are Qa , Qb ; the input is X ; the Moore output is Y ; and the Mealy output is Z .
Show your work.

