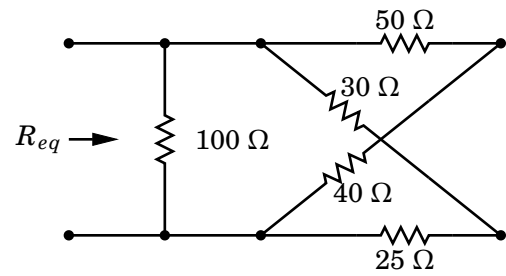



Give complete solutions. Closed book, closed notes. Show all you work, any unsupported answers will not be graded. No exchange of materials. Underline your answer or you lose half of your credit.

3.63, 4.20, 4.22, 4.35, 5.24, 5.47, 6.25, 6.22, 10.50 and 10.71


1. Find  $R_{eq}$  (10 pts).




2. Find  $i_1$  (10 pts).

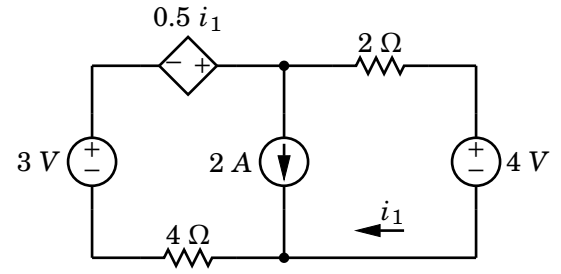

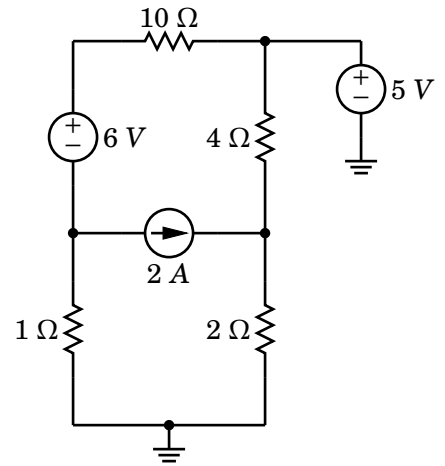
3. Find voltage difference across the  $4\ \Omega$  resistor (10 pts).




4. Find  $i_x$  (10 pts).

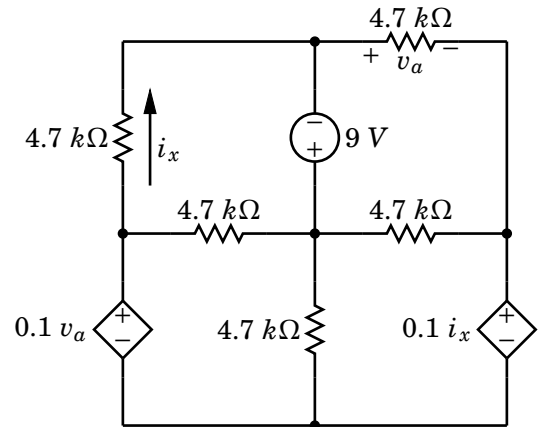

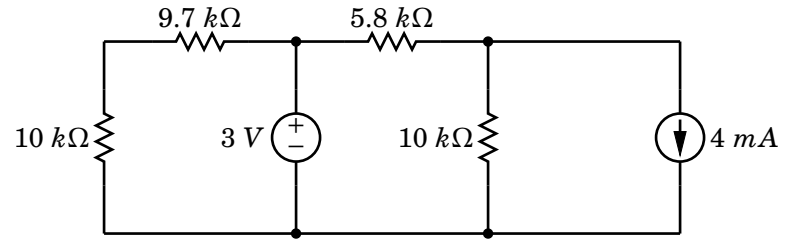
5. Determine the power dissipated by the  $5.8\text{ k}\Omega$  resistor (10 pts).



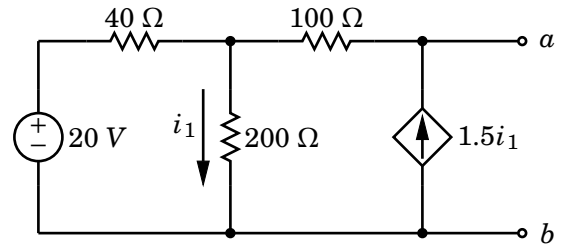
6. Find the equivalent circuit between a and b (10 pts).



7. Find  $v_{out}$  (10 pts).

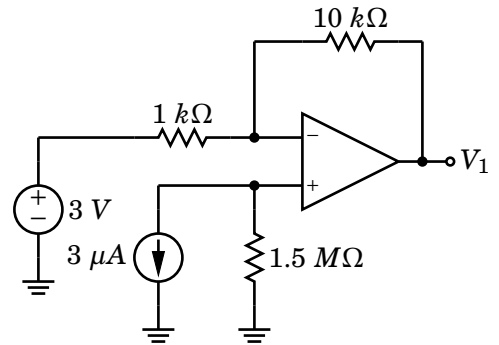


8. Find  $v_{out}$  (10 pts).

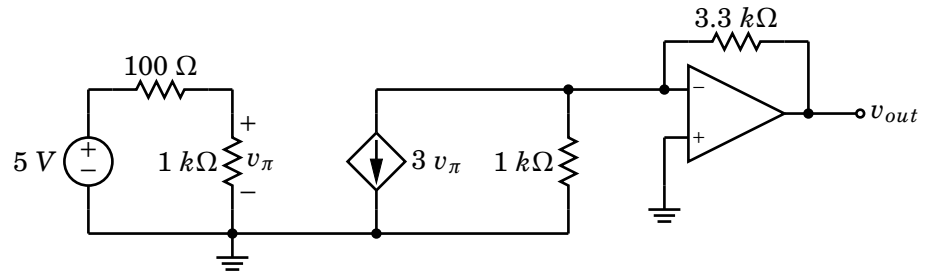



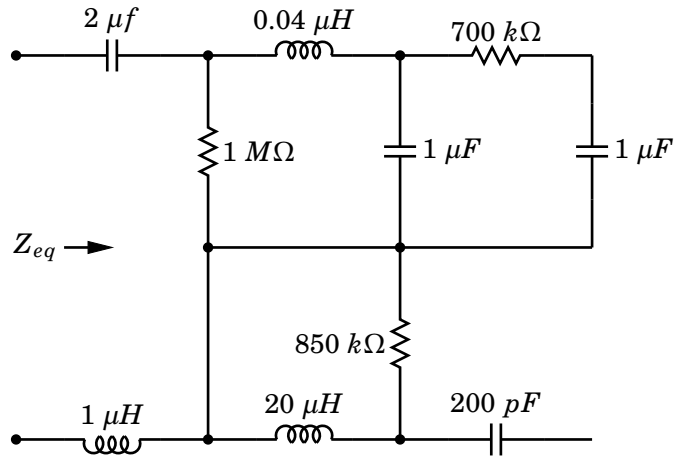9. Find the impedance if  $\omega = 1 \text{ MHz}$  (10 pts).



10. Find the current through the  $5\ \Omega$  resistor (10 pts).

